



# Table of contents

Introduction	11
About the author	13
<b>1 An introduction to the specifications of thermionic valves</b>	<b>15</b>
1.1 The numbering system of the pins of the valve base	16
1.2 The basic elements of the valve	16
1.3 The getter and the poisoned cathode	18
1.4 Determination of the valve characteristics	19
1.5 The valve characteristics	21
1.6 Valve specifications considered in a broader framework	23
1.7 Calculating $K$ and $D_a$	24
1.8 The limits of the Child-Langmuir equation	26
1.9 Valve models: discussions	28
1.10 'Fitting' the Child-Langmuir equation	29
1.11 The application of the $K/D_a$ -model	32
1.12 Tetrodes and pentodes	36
1.13 The specification of pentodes	39
1.14 Pentodes and Child-Langmuir-Compton	40
1.15 Calculation of the characteristics	44
1.16 The application of the $K/D_a$ -model for pentodes	48
1.17 Summary of chapter 1	54
1.18 Bibliography of chapter 1	54
<b>2 The output transformer: dimensioning the primary winding</b>	<b>56</b>
2.1 The optimum SE operation point of a triode	56
2.2 The SE-triode in a practical setup	59
2.3 The optimum SE-adjustment of a pentode	64
2.4 Transformers for push-pull amplifiers	66

2.5	The calculation of the current differences	68
2.6	The triode construction of B.J. Thomson	69
2.7	The pentode in class-A- & AB-configuration	79
2.8	Summary of chapter 2	86
2.9	Bibliography of chapter 2	86
<b>3</b>	<b>Special coupling techniques between the valves and the transformer</b>	<b>87</b>
3.1	The general coupling model	87
3.2	Testing the coupling model	93
3.3	Pentode based push-pull power amplifier	96
3.4	The ultra-linear push-pull power amplifier	100
3.5	Triode push-pull power amplifier	104
3.6	Optimising the triode push-pull amplifier	106
3.7	The cathode plus screen grid coupling: calculations	110
3.8	$\Gamma = 0.1$ -cathode negative feedback, $x = -1$ -screen grid positive feedback	111
3.9	$\Gamma = 0.1$ -cathode negative feedback and $x = -0.33$ screen grid positive feedback: the Super Pentode circuit <sup>®©</sup>	115
3.10	$\Gamma = 0.1$ -cathode negative feedback: the CFB-circuit	119
3.11	$\Gamma = 0.1$ -cathode- and $x = 0.33$ screen grid negative feedback: the super triode circuit <sup>®©</sup>	122
3.12	$\Gamma = 0.1$ -cathode- and $x = 1$ screengrid negative feedback	124
3.13	The "Unity Coupled" circuit	126
3.14	The cathode-follower push-pull end stage	132
3.15	Conclusion of chapter 3	135
3.16	Bibliography of chapter 3	136
<b>4</b>	<b>Valve amplifiers in the frequency domain</b>	<b>137</b>
4.1	Introduction to the frequency domain	137
4.2	The input stage in the frequency domain	143
4.3	The input stage at the middle frequencies	144
4.4	The input stage at low frequencies	146
4.5	The input stage at high frequencies	148
4.6	The equivalent model of the input stage	149
4.7	Drive stages and phase splitters	150
4.8	The equivalent model of the power valves	151
4.9	The equivalent schematic of the transformer	152
4.10	The transfer function of the power valves and the output transformer	154
4.11	The $-3$ dB frequency range	156

4.12	Calculation examples	158
4.13	The tuning of the output transformer	163
4.14	The influence of $C_k$ in SE power amplifiers	165
4.15	A closer examination of the Q-factor	168
4.16	The low frequency behaviour of an amplifier	174
4.17	Summary of chapter 4	181
4.18	Literature of chapter 4	182
<b>5</b>	<b>Feedback</b>	<b>185</b>
5.1	Negative voltage feedback	186
5.2	Current feedback	191
5.3	The combination of V-I-feedback	194
5.4	Feedback and stability	197
5.5	Negative feedback and sound	210
5.6	Literature of Chapter 5	222
<b>6</b>	<b>The QUAD II power amplifier</b>	<b>224</b>
6.1	The history	224
6.2	The restoration	226
6.3	The 'acoustical' circuit	228
6.4	Static and dynamic characteristics	230
6.5	The transfer function	234
6.6	Conclusion and recapitulation	237
6.7	Literature of chapter 6	237
<b>7</b>	<b>Le Miracle</b>	<b>239</b>
7.1	Guiding principles	241
7.2	The input stage and the pre-amplifier	242
7.3	The phase splitter and the driving stages	243
7.4	The power valves and the output transformer	244
7.5	The open-loop transfer function	246
7.6	Infinite damping factor?	247
7.7	Listening experiences	249
7.8	Conclusion	250
7.9	Literature of chapter 7	251
<b>8</b>	<b>The super-pentode / super-triode amplifier SPT-70</b>	<b>252</b>
8.1	The story of the challenge	252
8.2	The input pre-amplifier and the phase splitter B5	254
8.3	The pre-amplifier B4 and the cathode follower B3	258
8.4	The measurement values of the driving stage	260
8.5	The power valves and the output transformer	261

8.6	The power supply	262
8.7	The main power supply $V_0 = 450\text{ V}$	265
8.8	The stabilised power supply $V_1$ and $f_2$	266
8.9	The stabilised negative power supply $V_n$	267
8.10	The power supply for the safety circuits	268
8.11	The idling current of the power valves	269
8.12	A warning for the DIY-er	270
8.13	Measurements and conclusion	270
8.14	Part lists	271
<b>9</b>	<b>The universal amplifier and output transformer</b>	<b>277</b>
9.1	Basic questions	277
9.2	The principle of the valve amplifier	277
9.3	Specifications of a universal transformer	280
9.4	The universal output transformer	285
9.5	The universal power transformer	288
9.6	The schematic of the universal amplifier and power supply	288
9.7	Twenty amplifiers: the results	292
9.8	Calculating the local negative feedback	299
9.9	Local negative feedback with resistors	302
9.10	The guitar version of circuits 19 ... 20	307
9.11	Tips for the DIY-er	307
<b>10</b>	<b>Guitar amplifier 40W74-2</b>	<b>311</b>
10.1	A little bit history	311
10.2	A bird's eye view of the amplifier	313
10.3	The pre-amplifier	315
10.4	The main amplifier and the power supply	315
10.5	Literature of chapter 10	318
<b>11</b>	<b>The mini-triode amplifier MTV-10</b>	<b>319</b>
11.1	History	319
11.2	About the 6BX7-GT	322
11.3	The MTV-10 explained	323
11.4	The power supply	328
11.5	Concluding remarks	328
11.6	Literature chapter 11	330
<b>12</b>	<b>The 'Vanderveen auto-bias-secrets'</b>	<b>331</b>
12.1	Inventions and business	331
12.2	Standard auto-bias methods	332

12.3	How equal quiescent currents should be?	334
12.4	An overview of the inventions of others	335
12.5	The Vanderveen auto-bias circuit	339
12.6	Advantages and disadvantages	342
12.7	Literature of chapter 12	343
<b>13</b>	<b>The MCML05 valve pre-amplifier</b>	<b>344</b>
13.1	Block schematic of the MCML05	344
13.2	The MC-10 step-up transformer	345
13.3	The RIAA preamplifier	354
13.4	The line preamplifier	365
13.5	The power supply	369
<b>14</b>	<b>Valve amplifiers and electrostatic loudspeakers</b>	<b>375</b>
14.1	My first ESL	375
14.2	The principle of ESL	376
14.3	Simplified ESL-concept	378
14.4	The DC-offset problems	379
14.5	Between 20 Hz and 100 Hz	381
14.6	Between 100 Hz and 5000 Hz	383
14.7	The ESL-behaviour above 5 kHz	386
14.8	Balancing on the edge	389
14.9	The super-ESL-OPT-transformer?	390
14.10	Parameters of standard ESL-transformers	393
14.11	Summary	394
14.12	Literature chapter 14	394
<b>15</b>	<b>Something extra I wanted to tell you</b>	<b>395</b>
15.1	Symmetrical inputs	395
15.2	Symmetrical negative feedback	398
15.3	Speaking about damping	399
15.4	The bass-reflex port	403
15.5	Microphone rumble filter	404
15.6	Regulating from triode to pentode mode	405
15.7	Regulating from push-pull to SE	407
15.8	The DC-blocker	408
15.9	Conclusion	409
15.10	Literature of chapter 15	409
	Bibliography	411
	Where to obtain the Vanderveen transformers, specialist modules and services	416