
Table of Contents

Introduction	5
About the Author	6
1 Historical Background of Transconductance	9
2 Basic Principle of Transconductance	11
3 Why Is DC Coupling Necessary?	15
3-1: The prototype amplifier.	15
3-2: General characteristics of the prototype amplifier	18
3-3: Local negative feedback over filters	20
3-4: Why is DC coupling required?	21
4 Vanderveen Transie: DC-coupled SE Amplifiers.	23
4-1: Converting the one-tube amp into the Vanderveen Transie 1.	26
4-2: Measured performance of the Vanderveen Transie 1.	29
4-3: Subjective assessment of the Transie 1	34
4-4: A bit more power with the Transie 2.	34
5 Strict Requirements for Trans	37
5-1: Requirements for the output transformer	37
5-2: Requirements for the voltage-controlled current source	39
5-3: DC coupling and autobias settings	39
5-4: Output stage: pentode, ultra-linear or triode?	39
5-5: Component matching	40
6 Trans Test with Opamp Current Source	43
6-1: Basic design with opamp current source	43
6-2: Implementation of current source A and current sink B	44
6-3: Active autobias circuit.	46
6-4: Trans circuit for each output tube.	47
6-5: The complete push-pull Trans amplifier.	48
6-6: Conclusion and outlook.	52
7 Vanderveen Trans-30 Tube Amplifier	55
7-1: Basic design of the Vanderveen Trans-30	55
7-2: Trans circuit for each output tube.	56

7-3: Trans-30 autobias circuit. 57

7-4: The complete Vanderveen Trans-30 circuit 59

7-5: Objective performance figures 61

7-6: Subjective results 65

7-7: Postscript on the Vanderveen Trans-30. 66

8 A Deeper Analysis of Trans 67

8-1: About distortion in output transformers 67

8-2: Is PPP an alternative to Trans? 69

8-3: Characteristics of Trans output tubes 72

8-4: Remarkable high-frequency behavior 75

8-5: Local versus overall negative feedback 78

9 Epilog and Conclusions 81

10 Appendix 10-A: Pierre Toulezet on Transformer Distortion. 83

Appendix 10-B: Pierre Toulezet on PPP Amplifiers 87

11 References 101

Contact Information and Resources 103