

Audio Power Amplifiers – towards inherently linear amplifiers

Arto Kolinummi

Table of Contents

Abstract

Preface iii

Table of Contents

Abbreviations and Symbols

1	Introduction
1.1	Objectives of this study
1.1.1	The first phase of the study
1.1.2	The second phase of the study
1.2	Contents outline
1.3	Acknowledgements
2	Distortion measurement
2.1	Distortion modeling
2.2	Sources of distortion
2.3	Harmonic and intermodulation distortion
2.4	Dynamic distortion measurement
2.5	Distortion tests comparison
2.6	Difference tests
2.7	Measurements with subjective correction
2.8	Summary
3	Sources of dynamic distortion
3.1	Thermal distortion
3.2	Thermal effect on harmonic distortion
3.3	Power supply and speaker load dynamic distortion
3.3.1	Loudspeaker load
3.3.1.1	Speaker impedance
3.3.1.2	Nonlinearity of the speaker parameters
3.3.1.3	Transient impedance of the speaker
3.3.1.4	Interface intermodulation
3.3.1.5	Voltage or current drive
3.3.2	SOAR protection
3.3.3	Power supply
3.3.3.1	Supply voltage filtering
3.3.3.2	Supply currents in class-A and class-B biasing
3.4	Other error sources in audio system
3.3.4.1	Cabling
3.3.4.2	Dielectric absorption
3.3.4.3	Distortion in passive components
3.3.4.4	Contact distortion
3.5	Conclusions
4	Error correction methods
4.1	Principles of error correction
4.2	Negative feedback

- 4.3 Slew rate limiting
- 4.4 Internal overshoot
- 4.5 Loop compensation
 - 4.5.1 Lag (Miller) compensation
 - 4.5.2 Right half-plane zero
 - 4.5.3 Compensation methods affecting feedback factor
 - 4.5.4 Load dependent compensation
 - 4.5.5 Multipole compensation
 - 4.5.6 Nested feedback and cascaded amplifiers
- 4.6 Increase in high order harmonics
- 4.7 Error feedback and error feedforward
 - 4.7.1 EFB topologies
 - 4.7.2 Active negative feedback ANFB
 - 4.7.3 EFF topologies
 - 4.7.4 Error take-off
- 4.8 Summary

- 5 Transistor operation and linearity
 - 5.1 BJT operation basics
 - 5.1.1 Emitter degeneration
 - 5.2 Cascode and bootstrap
 - 5.2.1 Cascode circuits
 - 5.2.2 Bootstrap circuits
 - 5.3 Basic building blocks
 - 5.3.1 Current sources
 - 5.3.2 Current mirrors
 - 5.4 Thermal distortion
 - 5.5 The Complementary Feedback Pair
 - 5.6 Summary

- 6 Gain stages
 - 6.1 Input stages
 - 6.1.1 Differential pairs
 - 6.1.1.1 Emitter degeneration in differential pair
 - 6.1.1.2 Input differential impedance of the differential pair
 - 6.1.1.3 Common mode voltage and bootstrap
 - 6.1.2 Device matching
 - 6.1.3 Methods to improve differential pair linearity
 - 6.1.3.1 EFF and EFB correction in differential pairs
 - 6.1.3.2 Using the CFP in differential amplifiers
 - 6.1.3.3 Using JFETs in differential amplifiers
 - 6.1.4 Complementary symmetric input topologies
 - 6.2 Intermediate stages
 - 6.2.1 Single-ended input stage loading.
 - 6.2.2 Active input stage structures 1
 - 6.2.2.1 AC-bootstrap loading
 - 6.2.2.2 Current source loading
 - 6.2.2.3 Current mirror loading
 - 6.2.3 The Voltage Amplifier Stage
 - 6.2.4 The Differential VAS
 - 6.2.5 Complementary Symmetrical Input Stage VAS
 - 6.2.6 The Folded Cascode
 - 6.2.7 Current feedback structures

6.2.8	Gain Stage Open Loop Performance
6.2.9	Novel bootstrapped folded cascode gain stage
6.2.9.1	DC-offset, component mismatch and thermal performance
6.2.9.2	PSRR, CMRR
6.2.9.3	Slew Rate
6.3	Summary
7	Output stages
7.1	Evolution of transistor output stages
7.2	Driver stages for the output stage
7.3	Output stage linearity
7.3.1	Large signal current nonlinearities
7.3.2	Gm-doubling distortion
7.3.2.1	Effects of emitter and base resistances on gm-doubling
7.3.3	Optimal bias versus class-AB bias
7.3.4	Paralleling output transistors
7.3.5	Emitter and source follower parasitic oscillation
7.4	Constant voltage biasing
7.5	Switching distortion
7.5.1	Non-switching power stages
7.5.2	Sliding bias
7.6	Optimizing the output stage linearity
7.7	Techniques to increase efficiency in class-A and –AB amplifiers
7.8	Output stage error correction
7.8.1	EFF correction in power stage
7.8.2	Global error corrector structures
7.8.2.1	Current-dumping
7.8.3	Current bootstrapping
7.8.4	Error Feedback Correction in power stages
7.8.5	Novel error correction circuits
7.9	Summary
8	Realisations
8.1	The Global Feedback amplifier
8.2	Zero Feedback and Error Corrector designs
8.2.1	The output stage
8.2.2	The gain stage
8.2.3	Zero Feedback amplifier version 1
8.2.4	Zero-Feedback amplifier version 2
8.3	Listening tests
9	Conclusions
9.1	Error measurements and error sources
9.2	Error correction methods
9.3	Internally linear circuit structures
9.4	Realisations
10	References