

---

<b>Contents .....</b>	<b>3</b>
<b>Biography .....</b>	<b>7</b>
<b>Preface .....</b>	<b>8</b>
<b>Chapter 1: The Universe of Video .....</b>	<b>12</b>
<b>Chapter 2: Television Standards .....</b>	<b>15</b>
2.1 History and Prehistory of Television.....	15
2.2 What standard to choose?.....	21
2.3 The waveforms of synchronisms .....	23
2.3.1 Horizontal & Vertical pulses .....	24
2.3.2 Interlace 2:1 .....	25
2.3.3 Broad & Equalisation pulses.....	25
2.3.4 Vertical frequency .....	26
2.3.5 Aspect ratio .....	27
2.3.6 Video Bandwidth .....	28
2.4 Sync Pulse Generators (SPGs).....	29
2.4.1 Single chip SPGs.....	30
2.4.2 Multiple chip SPGs.....	35
2.4.3 Non-standard SPGs.....	39
2.5 Sync extraction.....	40
2.6 A curious television scanning alternative! .....	44
<b>Chapter 3: Colour Television Standard Systems .....</b>	<b>46</b>
3.1 The Human Eye .....	46
3.2 From eye to its electronic representation.....	47
3.3 NTSC & PAL Encoding .....	52
3.4 SECAM System .....	59
3.5 The relative merits and demerits of TV standards.....	60
3.5.1 NTSC/525-lines pros .....	61
3.5.2 NTSC/525-lines cons .....	61
3.5.3 PAL/625-lines pros.....	61
3.5.4 PAL/625-lines cons .....	62
3.5.5 SECAM/625-lines pros .....	62

---

3.5.6	SECAM/625-lines cons.....	62
3.6	Other analogue colour television systems .....	64
3.7	Colour Encoders.....	65
3.7.1	Digital Inputs Encoder Chips.....	65
3.7.2	Analogue Input Encoder Chips .....	68
3.8	NTSC & PAL Colour Decoding.....	76
3.9	SECAM decoding.....	79
3.10	Colour Decoder Chips .....	81
3.10.1	Analogue Decoders.....	81
3.10.2	SECAM decoders .....	89
3.10.3	Digital & Pseudo-Digital Decoders.....	91
3.10.4	Digivision TV chipset.....	94
3.11	Video conversion .....	96
3.11.1	From PAL S-Video to CVBS and vice versa.....	97
3.11.2	From YUV to RGB and vice versa .....	98
3.12	Some final considerations .....	99
<b>Chapter 4: Pattern &amp; monoscope generators.....</b>		<b>101</b>
4.1	The Colour Test Pattern Bars Generator .....	102
4.2	Patterns for TV set calibration.....	108
4.3	Multiburst Generator.....	110
4.4	An automatic RGB Colour Changer.....	113
4.5	Test Cards & Monoscopes .....	114
4.6	Software based Test Card Generators.....	117
4.7	Two final remarks .....	121
<b>Chapter 5: Television display systems.....</b>		<b>124</b>
5.1	A little bit of history... ..	124
5.2	Display Devices.....	126
5.2.1	The Oscilloscope.....	127
5.2.2	The Waveform Monitor.....	130
5.2.3	A LED Oscilloscope.....	131
5.2.4	The Vectorscope.....	133
5.2.5	The Baird's 'Radiovision', the first industrial mechanical television set .....	134
5.2.6	The Cathode Ray Tube (CRT) or Kinescope .....	135
5.2.7	Other types of CRTs.....	142

---

5.2.8	The Field Emission Display (FED) .....	143
5.2.9	The Surface-conduction Electron-emitter Display (SED) .....	144
5.2.10	The Liquid Crystal Display (LCD) .....	144
5.2.11	The Active Matrix Liquid Crystal Display (AMLCD) .....	145
5.2.12	The HDR-TV Display .....	146
5.2.13	The Plasma Display Panel (PDP) .....	146
5.2.14	The Organic Light Emitting Diode (OLED) Display .....	147
5.2.15	The Thick-Film Dielectric Electroluminescent (TDEL) Display .....	148
5.2.16	The WOWvx Display .....	149
5.2.17	The Virtual Retinal Display (VRD) .....	150
5.2.18	Large screen displays .....	150
5.2.19	Multiple screen displays .....	153
5.3	Things to Think About .....	154

**Chapter 6: Video Cameras..... 156**

6.1	Tube-based Camera Devices .....	156
6.1.1	The first experimental camera tubes .....	157
6.1.2	Further developments on camera tubes .....	158
6.1.3	1, 2, 3 or even 4-tube Colour Cameras .....	161
6.1.4	Pickup tube features .....	164
6.2	Solid-state Pickup Devices .....	165
6.2.1	The CCD (Charge Coupled Device) .....	165
6.2.2	CMOS image sensors .....	169
6.3	Features common to all Cameras .....	170
6.4	Some final considerations .....	172

**Chapter 7: Video recorder systems..... 174**

7.1	Video recording chronological history .....	174
7.2	Video cassette recorder mechanisms .....	183
7.3	Magnetic playback and recording techniques .....	187
7.4	Footage transferring .....	189
7.5	Analogue Anticopy Protection .....	191
7.5.1	How does the anticopy system work? .....	192
7.5.2	How to eliminate protection pulses .....	193
7.5.3	Description of the circuit .....	193
7.5.4	The output stage & Power Supply .....	195

---

7.5.5	Assembling & Soldering.....	195
7.5.6	Calibration .....	196
7.5.7	Inside a box.....	197
7.5.8	Bad thoughts.....	198
7.6	Some conclusive considerations .....	198
<b>To be continued .....</b>		<b>200</b>
<b>Bibliography .....</b>		<b>201</b>
<b>Index .....</b>		<b>205</b>